

Logic design

Binary operation

- ▶ Many object and phenomena can represent binary data

有 無 上 下 黑 白 真 偽 勝 負
 北 南 負 正 錯 對 陽 陰 關 開 1 0

- ▶ Many mathematical concepts for binary data have similar structure

- ▶ Set operation:
 - ▶ Basic element: Empty set/Universal set
 - ▶ Operation: UNION, INTERSECTION, COMPLEMENT
- ▶ Logic operation:
 - ▶ Basic element: True/False
 - ▶ Operation: AND, OR, NOT,...

- ▶ More of those mathematical properties will be taught in Discrete Math

Boolean operation

- ▶ Any operation that manipulates one or more true/false values
 - ▶ Can be used to operate on bits
- ▶ Specific operations
 - ▶ AND
 - ▶ OR
 - ▶ XOR
 - ▶ NOT
- ▶ Gates are devices that produce the output of a Boolean operation when given the operation's input values

AND



- ▶ The AND Operation

| | | | | |
|-----|---|---|---|---|
| | 0 | 1 | 0 | 1 |
| AND | 0 | 0 | 1 | 1 |
| | 0 | 0 | 0 | 1 |

OR

▶ The OR Operation

| | | | |
|--|--|--|--|
| $\begin{array}{r} 0 \\ \text{OR } 0 \\ \hline 0 \end{array}$ | $\begin{array}{r} 1 \\ \text{OR } 0 \\ \hline 1 \end{array}$ | $\begin{array}{r} 0 \\ \text{OR } 1 \\ \hline 1 \end{array}$ | $\begin{array}{r} 1 \\ \text{OR } 1 \\ \hline 1 \end{array}$ |
|--|--|--|--|

XOR (eXclusive OR)

▶ The OR Operation

| | | | |
|---|---|---|---|
| $\begin{array}{r} 0 \\ \text{XOR } 0 \\ \hline 0 \end{array}$ | $\begin{array}{r} 1 \\ \text{XOR } 0 \\ \hline 1 \end{array}$ | $\begin{array}{r} 0 \\ \text{XOR } 1 \\ \hline 1 \end{array}$ | $\begin{array}{r} 1 \\ \text{XOR } 1 \\ \hline 0 \end{array}$ |
|---|---|---|---|

NOT

▶ The NOT Operation

| | |
|--|--|
| $\begin{array}{r} \text{NOT } 0 \\ \hline 1 \end{array}$ | $\begin{array}{r} \text{NOT } 1 \\ \hline 0 \end{array}$ |
|--|--|

Truth table


▶ Enumerates all the input combinations and the corresponding output of Boolean operations

▶ Four commonly used Boolean operators

| Input | Output | Input | Output | Input | Output | Input | Output |
|-------|--------|---------|--------|-------|---------|-------|--------|
| A | B | A.and.B | A.or.B | A | A.xor.B | A | Not A |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 | | |
| 1 | 1 | 1 | 1 | 1 | 0 | | |

Boolean functions

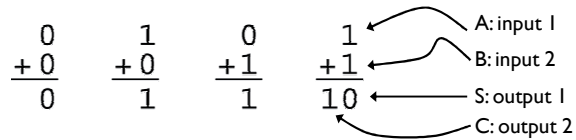- ▶ Almost all binary operations of computers can be carried out by logic gates
- ▶ Example: One bit adder
 - ▶ Two inputs and two outputs (S: sum, C: carry out)




Implementation of an one bit adder

- The truth table of an one-bit adder

| A | B | S | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

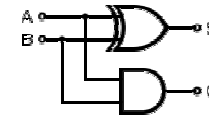
- Compare it to the truth table of Boolean function AND, OR, XOR, NOT
 - $S = A .XOR. B$
 - $C = A .AND. B$



▶ More of those will be taught in '邏輯設計'.



One bit full adder

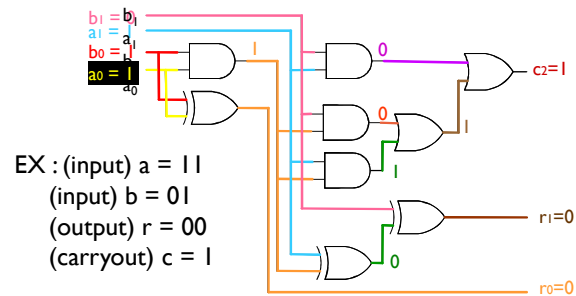- ▶ Equations : (sum) $s_i = a_i \oplus b_i \oplus c_i$
(carry out); $c_{i+1} = ab_i + ac_i + bc_i$



Flip-flops

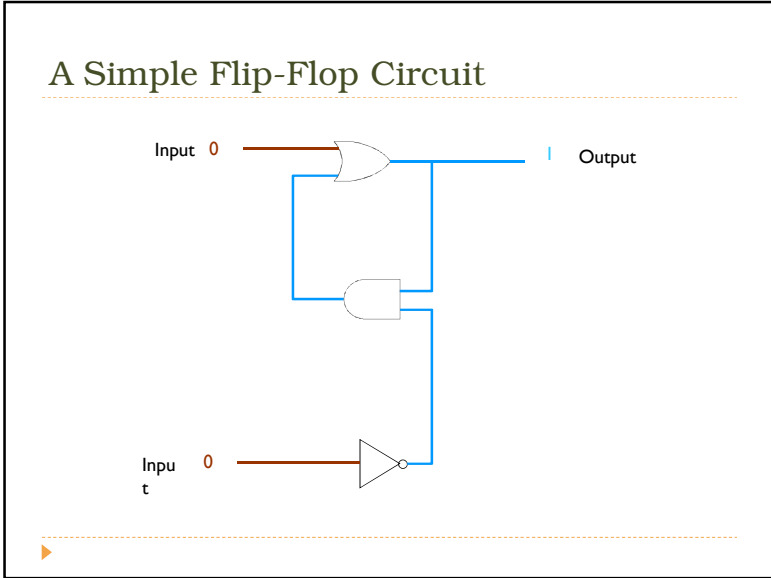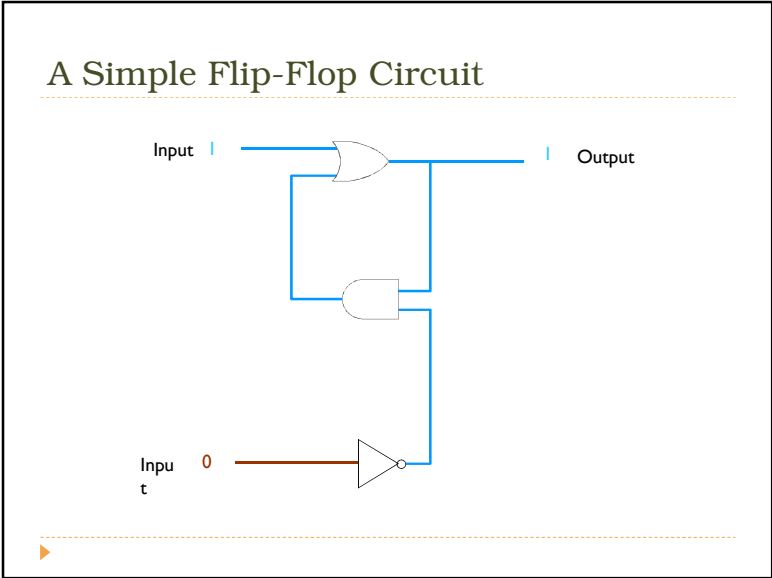- ▶ **Flip-flop** = a circuit built from gates that can store one bit of data.
 - ▶ Has an input line which sets its stored value to 1
 - ▶ Has an input line which sets its stored value to 0
 - ▶ While both input lines are 0, the most recently stored value is preserved
- ▶ A flip-flop is ideal for the storage of a bit within a computer
 - ▶ A flip-flop loses data when its power is turned off



What can be a gate?



- ▶ LEGO's "mechanical gates"
 - ▶ The AND gate

Circuit gates

- ▶ Can we flip the switches without hands?


Electronic switch

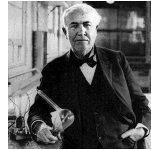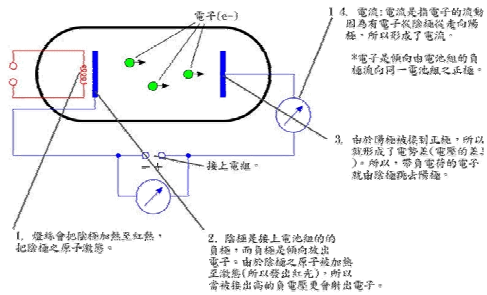- ▶ The earliest one is the vacuum tube
 - ▶ 1884, Thomas Edison




Transistor

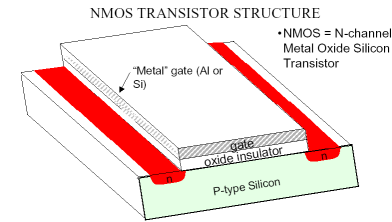- ▶ The problems of vacuum tubes are slow, large, expensive, and easy to break.
- ▶ Transistor can make it faster, smaller, and more robust.




Transistors for logic gates

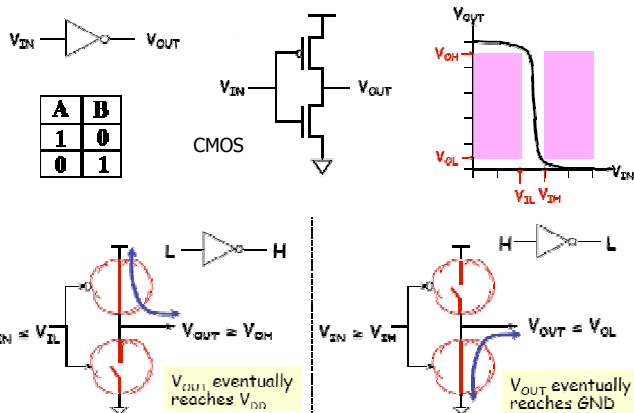

▶ More of those will be taught in "電子電路"

Integrated circuit (IC)

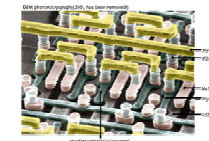- ▶ An electronic circuit consisted of transistors and other components in the thin substrate of semiconductor material.
- ▶ Also known as **IC**, **microchip**, or **chip**.
- ▶ Invented by Jack Kilby and Robert Noyce
 - ▶ 2000 Nobel Prize in Physics
- ▶ **VLSI**: Very-Large-Scale IC
 - ▶ More than million transistors



▶ More in "VLSI設計"